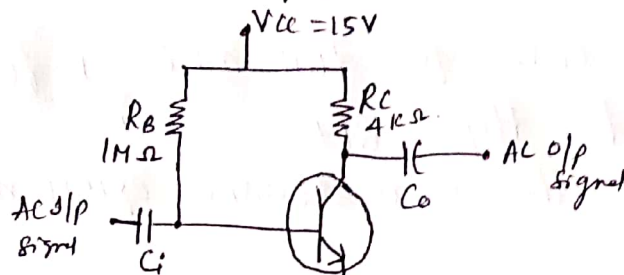


ADE Model Question paper II.

Module-1.

1a) Explain Construction of LED? 6M

b) for the fixed-bias circuit of h_{FE} , determine the operating point (given the transistor gain $\beta = 100$, $V_{BE} = 0.7V$). Also draw the load line for the circuit. 8M.



c) Explain opamp application as peak detector? 6M.
OR.

2a) Explain opamp application as Schmitt trigger? 6M.

b) Explain voltage to current converter? 6M.

c) Explain R-2R ladder circuit? 8M.

MODULE-2.

3a) Simplify using K-map $F(A, B, C, D) = \sum m(1, 3, 5, 7, 9) + \sum d(6, 12, 13)$? 6M.

b) Write SOP + POS for $F(A, B, C, D) = \prod M(1, 5, 6, 7, 9, 12, 13, 14)$? 8M.

c) Apply EVM method $F(W, X, Y, Z) =$

$\sum m(1, 3, 5, 7, 13, 14, 15, 16)$? 6M.

OR.

4a) Explain Quine's method with example? 6M.

b) Find a min SOP using Quine's McCluskey method.

$F(A, B, C, D) = \sum m(1, 3, 4, 5, 6, 7, 10, 12, 13) + \sum d(2, 9, 15)$
14M.

MODULE-3.

5a) Realize $F_1(A, B, C) = \sum m(0, 2, 3, 4, 5) + F_2(A, B, C) = \sum m(0, 2, 3)$ using only 2-input NAND gate + inverter? 8M. 4M.

b) Explain the working of Simulator for Combinational Logic? 6M.

c) Realize $F(W, X, Y, Z) = \sum m(1, 2, 5, 6, 8, 9, 10, 11, 14, 15)$ using 8:1 MUX? 6M.

OR.

6a) Realize $F_1(a,b,c) = \sum m(0,3,5)$, $F_2(a,b,c) = \sum m(1,5,6)$, &
 $F_3(a,b,c) = \sum m(2,3)$ using 3:8 decoder? 6M.

b) Realize 7-segment decoder using PLA? 8M.

c) Write a note on programmable array logic? 6M.

MODULE-4

7a) Write a VHDL code for full-adder + full-subtractor? 8M.

b) Explain SR flip flop? 6M.

c) ~~Construct~~ Deduce the characteristic equation for D & T flip flop? 6M.

8a) Briefly explain OR packages + libraries in VHDL? 6M.

b) Convert JK flip flop to SR flip flop? 8M.

c) Explain edge-triggered JK flip flop? 6M.

MODULE-5

9a) Explain n-bit Parallel adder with accumulator? 6M.

b) Explain Johnson Counter? 6M.

c) Explain moore model + mealy model in brief? 8M.

OR.

10a) Design 3-bit up-down counter using D ff? 8M.

b) Draw state table diagram for serial adder? 6M.

c) Differentiate b/w moore + mealy model? 6M.