

--	--	--	--	--	--	--	--	--	--

**Third Semester B.E. Degree Examination, Jan./Feb. 2021**  
**Analog and Digital Electronics**


Time: 3 hrs.

Max. Marks: 100

*Note: Answer any FIVE full questions, choosing ONE full question from each module.*

**Module-1**

- 1 a. Explain the working principle of opto coupler with neat diagram. (06 Marks)  
 b. Derive an expression for collector current and collector emitter voltage of fixed bias circuit. (06 Marks)  
 c. For the circuit shown in Fig.Q.1(c), draw DC load line, use silicon transistor with  $\beta = 50$ ,  $V_{BE} = 0.7V$ . (08 Marks)

 **OR**

- 2 a. With the help of neat circuit diagram and wave form explain the working principle of relaxation oscillator. (10 Marks)  
 b. Explain current to voltage converter. (05 Marks)  
 c. Define voltage regulator. Explain adjustable voltage regulator. (05 Marks)

**Module-2**

- 3 a. Simplify the following function using K-map and obtain simplified Boolean expressions.  
 i)  $f_1(a, b, c, d) = \sum m(1, 3, 4, 5, 7, 10, 12)$   
 ii)  $f_2(a, b, c, d) = \sum m(5, 8, 9, 10, 11, 12, 13, 14, 15)$  (10 Marks)  
 b. Find all the prime implicants of function using Q-M method.  
 $f(a, b, c, d) = \sum m(0, 2, 3, 4, 8, 10, 12, 13, 14)$  (10 Marks)

**OR**

- 4 a. For the following function given use Q-M method and obtain simplified expression:  
 $f(a, b, c, d) = \sum m(7, 9, 12, 13, 14, 15) + dc(4, 11)$  (08 Marks)  
 b. With an example explain Petrik's method. (06 Marks)  
 c. For the given function determine minimal sum using MEV technique. Use d as MEV variable.  $f(a, b, c, d) = \sum m(3, 4, 5, 7, 8, 11, 12, 13, 15)$ . (06 Marks)

**Module-3**

- 5 a. Define static 1 – hazard. Explain how static 1-hazard can be detected and removed with an example. (08 Marks)  
 b. What is multiplexer and explain 8 to 1 mux with the help of logic diagram and corresponding expression. (06 Marks)  
 c. Explain the importance of three-state buffer. (06 Marks)

OR

- 6 a. Implement the following functions using 3:8 decoder  
 $f_1(a, b, c) = \sum m(0, 4, 6, 7)$   
 $f_2(a, b, c) = \sum m(1, 4, 5)$  (06 Marks)
- b. Implement the following Boolean functions using an appropriate PLA:  
 $f_1(a, b, c) = \sum m(0, 4, 7)$   
 $f_2(a, b, c) = \sum m(4, 6)$  (06 Marks)
- c. Realize a full adder using PAL. (08 Marks)

**Module-4**

- 7 a. Explain the structure of VHDL program. Write VHDL code for 4-bit parallel adder using full adder as component. (08 Marks)
- b. With necessary diagrams, Explain switch debouncing with an S-R latch. (06 Marks)
- c. Explain D flip-flop with the help of timing diagram. (06 Marks)

OR

- 8 a. Give the implementation of T-flip-flop from D flip-flop. (04 Marks)
- b. Explain master-slave J-K flip-flop operation. (08 Marks)
- c. Derive the characteristic equations for the following flip-flops:  
 i) S-R flip-flop  
 ii) D-flip flop  
 iii) T-flip-flop  
 iv) J-K flip-flop. (08 Marks)

**Module-5**

- 9 a. With neat sketch, explain the working principle of Serial Input Serial Output (SISO) shift register. (06 Marks)
- b. Design 3 bit synchronous binary counter using transition table of T-flip-flop (08 Marks)
- c. Explain how 4 bit register with data, load, clear and clock input is constructed using D-flip-flops. (06 Marks)

OR

- 10 a. With the help of state graph, state and transition table and timing diagram, explain sequential parity checker. (06 Marks)
- b. With the help of block diagram, explain the working principle of n-bit parallel adder with accumulator. (08 Marks)
- c. Analyze following Moore sequential circuit for an input sequence  $X = 01101$  and draw the timing diagram. (06 Marks)

 


Fig.Q.10(c)

\*\*\*\*\*